

Microprocessor Design

School of Computer Science and Electronic Engineering
University of Essex (UK)


CE339/CE869 - Lecture 7
Jan 2020

Outline

- Overview of A Microprocessor
- Datapath
- Control Unit
- Memory
- Lab ALU


Overview of A Microprocessor

 - The Von Neumann model of a computer consists of four main components: the input, the output, the memory, and the microprocessor.
- We are concentrating on the design of digital circuitry of the microprocessor, the memory, and other supporting digital logic circuits.
- The logic circuit for a microprocessor can be divided into two parts: **datapath** and **control unit**.




Datapath

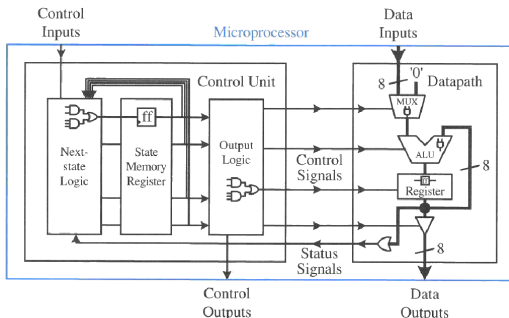- The datapath is responsible for the actual execution of all data operations performed by the microprocessor.
- The ALU and the register are connected together with multiplexers and data signal lines.
- In the following architecture, the output is connected to:
 - the right operand of the ALU.
 - an OR gate used as comparator for the test “not equal to 0”.
 - a tri-state buffer.



Control Unit

- The control unit controls all of the operations of the datapath and the operation of the entire microprocessor.
- It is a finite state machine (FSM) that executes by going from one state to another and there are only a finite number of state for the machine to go to.
- There are three parts:
 - the next-state logic - to determine what the next state should be.
 - the state memory - to remember the current state that the FSM is in.
 - the output logic - to generate the control signals for controlling the datapath.

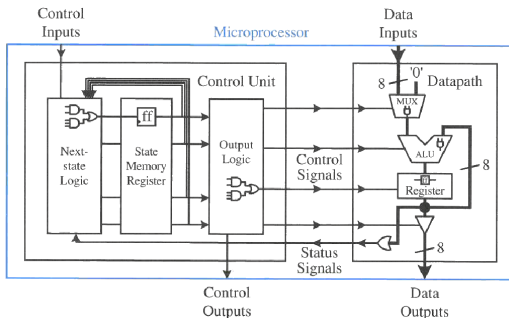


Outline

- Overview of A Microprocessor
- **Datapath**
- Control Unit
- Memory
- Lab ALU

Arithmetic Logic Unit (ALU)

Example of ALU:

 


s_2	s_1	s_0	Operation
0	0	0	Pass
0	0	1	AND
0	1	0	OR
0	1	1	NOT
1	0	0	Addition
1	0	1	Subtraction
1	1	0	Increment
1	1	1	Decrement

Arithmetic Logic Unit (ALU)

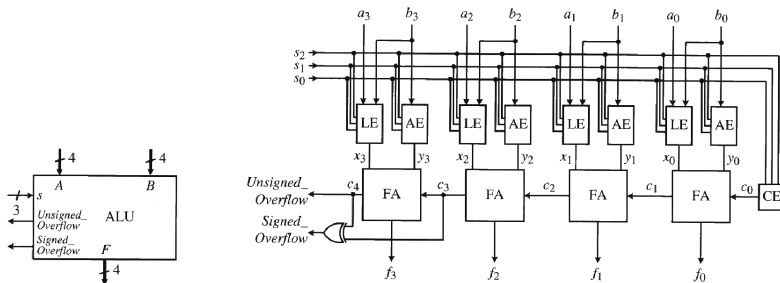Example of implementation:

- A four bit adder.
- The logic extender (LE) is for manipulating all logic operations.
- The arithmetic extender (AE) is for manipulating all arithmetic operations.
- The carry extender (CE) is for modifying the primary carry-in signal, so that arithmetic operations are performed correctly.



ALU Truth Table


Example of ALU truth table:

s_2	s_1	s_0	Operation	x_i (LE)	y_i (AE)	c_0 (CE)
0	0	0	Pass	a_i	0	0
0	0	1	AND	a_i AND b_i	0	0
0	1	0	OR	a_i OR b_i	0	0
0	1	1	NOT	a'_i	0	0
1	0	0	Addition	a_i	b_i	0
1	0	1	Subtraction	a_i	b'_i	1
1	1	0	Increment	a_i	0	1
1	1	1	Decrement	a_i	1	0

Tri-State Buffer

- It has three states 0, 1, and Z.
- The value Z represents a high-impedance state, which acts like a switch that is opened.
- It is used to connect several devices to the same bus.
- If two or more devices are connected directly to a bus without using tri-state buffer, signals will get corrupted on the bus.

B	C
0	Z
1	A

 

Tri-State VHDL


```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;

ENTITY TriStateBuffer IS PORT(
    E: IN STD_LOGIC;
    D: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
    Y: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
END TriStateBuffer;

ARCHITECTURE Behavioral OF TriStateBuffer IS
BEGIN
    Y <= D WHEN E = '1'
        ELSE (OTHERS=>'Z');
END Behavioral;
```

Register

 
- A register stores a multi-bit value, with enable (load), set, and clear inputs.
- A collection of D-latches, all controlled by a common WE.
- When $WE=1$, n -bit value D is written to register



Latch Inference

- Consider the incomplete **if** statement shown below (i.e. no else part!)
- What happens if the condition is tested and found to be false?
- In this case the value of Q should stay the same.
- Therefore a latch is required to store the value of Q.

 
```
if ENABLE = '1' then  
    Q <= D;  
end if;
```



- If the process is gated by a clock, a set of flip-flops (instead of latches) is inferred.

Register Files

- Register file: an **array of registers** in a CPU.
- Unlike SRAMs, it has **dedicated read and write ports** (ordinary SRAMs usually read and write through the same ports).
- It is usually used for the **source operands** and **destination** of the ALU and therefore it has one write port and two read ports.
- Since the ALU normally takes two input operands, the register file should be able to **output two values from two different locations** at the same time.
- Write is synchronous while read is often asynchronous**: in a single clock, data can be read, transformed and written back.

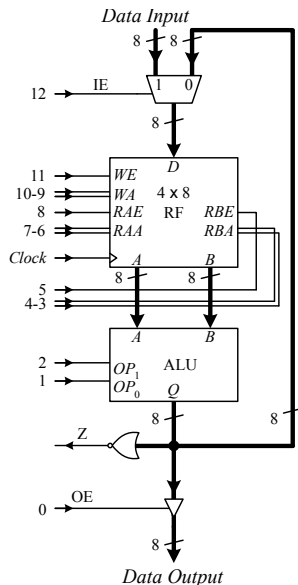

Dedicated Register File

- One write port and two read port register file.
- The read ports A and B are connected to the two input operands of the ALU.

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.NUMERIC_STD.all;

ENTITY regfile IS PORT (
    clk: IN STD_LOGIC;
    WE: IN STD_LOGIC;           — write enable
    WA: IN STD_LOGIC_VECTOR(2 DOWNTO 0); — write address
    RAE: IN STD_LOGIC;          — read port A enable
    RAA: IN STD_LOGIC_VECTOR(2 DOWNTO 0); — read port A address
    RBE: IN STD_LOGIC;          — read port B enable
    RBA: IN STD_LOGIC_VECTOR(2 DOWNTO 0); — read port B address
    input: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
    Aout, Bout: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
END regfile;

```

Dedicated Register File

```

ARCHITECTURE Behavioral of regfile IS
  SUBTYPE reg IS STD_LOGIC_VECTOR(7 DOWNTO 0);
  TYPE regArray IS ARRAY(0 TO 7) OF reg;
  SIGNAL RF: regArray;
BEGIN
  WritePort: PROCESS
  BEGIN
    WAIT UNTIL RISING_EDGE(clk);
    IF WE = '1' THEN
      RF(TO_INTEGER(UNSIGNED(WA))) <= input;
    END IF;
  END PROCESS;

  --ReadPortA
  Aout <= RF(TO_INTEGER(UNSIGNED(RAA))) WHEN RAE = '1'
    ELSE (OTHERS => '0');

  --ReadPortB
  Bout <= RF(TO_INTEGER(UNSIGNED(RBA))) WHEN RBE = '1'
    ELSE (OTHERS => '0');
END Behavioral;

```


Datapath Design


- A datapath consists of:
 - Functional units (adder, shifter, ALU, comparator, multiplexer, counter).
 - Registers.
 - Buses and tri-state buffer.
- The operations are determined by the control signals from the control unit.
- It must generate **status signals** from the comparators to the control unit (for jump instructions).
- Here we are concentrating on **dedicated datapath**. **General datapath** will be introduced in next lecture.

Dedicated Datapath: IF-THEN-ELSE

- Construct a 4-bit-wide dedicated datapath for solving the IF-THEN-ELSE algorithm

```

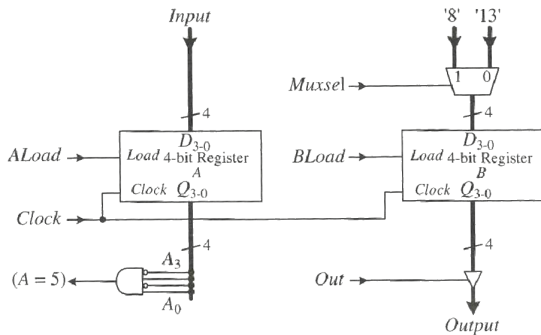INPUT A
IF (A = 5) THEN
    B = 8
ELSE
    B = 13
END IF
OUTPUT B
  
```



Dedicated Datapath: Control Word

- Control word has one bit for each control signal.
- Each control word takes one clock cycle to perform.
- By combining multiple control words together, the datapath performs the operations in the order given.

Control word	Instruction	Aload	Muxsel	Bload	Out
1	INPUT A	1	×	0	0
2	B = 8	0	1	1	0
3	B = 13	0	0	1	0
4	OUTPUT B	0	×	0	1


Outline

- Overview of A Microprocessor
- Datapath
- **Control Unit**
- Memory
- Lab ALU


Control Unit

- The **control unit** inside the microprocessor is a FSM.
- It includes the state memory, the next-state logic, and the output logic.
- By stepping through a sequence of states, it controls the operations of the datapath.
- It generates the control signals and controls the sequence of the instructions.
- A state is created for each control word and each state is executed in one clock cycle.

 IF-THEN-ELSE: State diagram and Next State Table




cur_state	next_state	
	(A=5)'	(A=5)
s_input	s_extra	s_extra
s_extra	s_notequal	s_equal
s_notequal	s_output	s_output
s_equal	s_output	s_output
s_output	s_output	s_output

 


IF-THEN-ELSE: Output, Control Words

Outputs
(control words):

cur_state	CW
s_input	1X00
s_extra	0X00
s_equal	0110
s_notequal	0010
s_output	0X01

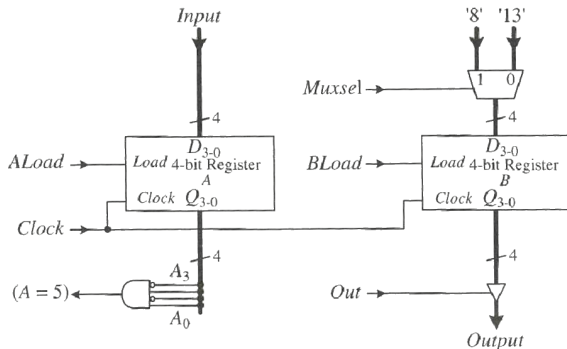

IF-THEN-ELSE: Control Unit's Schematics

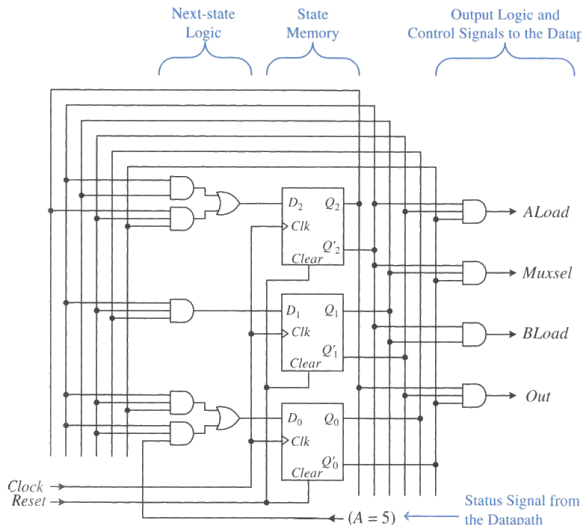

Outline



- Overview of A Microprocessor
- Datapath
- Control Unit
- **Memory**
- Lab ALU

Memory

- Two basic kinds of RAM (Random Access Memory)
 - Static RAM (SRAM)
 - Memory cell uses flip-flop to store bit;
 - Holds data as long as power supplied;
 - Fast.
 - Dynamic RAM (DRAM)
 - Memory cell uses MOS transistor and capacitor to store bit;
 - More compact than SRAM;
 - Slower but denser;
 - Must be periodically refreshed due to capacitor leak - word's cells refreshed when read;
 - Typical refresh rate $15.625\mu s$.
- Non-volatile memories: ROM, EPROM, flash, ...


RAM: “Random-Access” Memory

  - A common data bus for both reading from and writing to data to the memory.
- Just one data port.
- The number of address lines (n) is dependent on how many locations are in the memory chip, usually a power of 2.
- Chip enable (CE)
- One bit memory cell



Static RAM

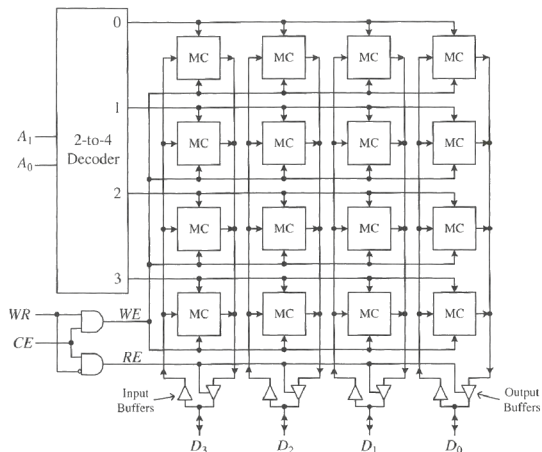- 4×4 static RAM chip.
- Each row forms a single storage location.
- The number of memory cells in a row determines the bit width of each location.
- A 2-to-4 decoder is used to decode the four address location.



RAM VHDL Entity

- 16×4 RAM with 4 address lines and 4 data lines.
- The bi-directional data port is declared as INOUT - can be read from and written to.
- The actual memory content is stored in the variable mem, which is an array of type STD_LOGIC_VECTOR.

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.all;  
USE IEEE.NUMERIC_STD.all;  
  
ENTITY memory IS PORT(  
    CE, WR: IN STD_LOGIC;      -- chip enable, write enable  
    A: IN STD_LOGIC_VECTOR(3 DOWNTO 0); -- address  
    D: INOUT STD_LOGIC_VECTOR(3 DOWNTO 0)); -- data  
END memory;
```

RAM VHDL Architecture

```

ARCHITECTURE Behavioral OF memory IS
BEGIN
  PROCESS(CE,WR)
    SUBTYPE cell IS STD_LOGIC_VECTOR(3 DOWNT0 0);
    TYPE memArray IS ARRAY(0 TO 15) OF cell;
    VARIABLE mem: memArray;
  BEGIN
    IF CE = '1' AND WR = '0' THEN      -- read
      D <= mem(TO_INTEGER(UNSIGNED(A)));
    ELSIF CE = '1' AND WR = '1' THEN    -- write
      mem(TO_INTEGER(UNSIGNED(A))) := D;
    ELSE -- not enabled or invalid
      D <= (OTHERS=>'Z');
    END IF;
  END PROCESS;
END Behavioral;

```

RAM VHDL Architecture

```

ARCHITECTURE Behavioral OF memory IS
BEGIN
    PROCESS(CE,WR)
        SUBTYPE cell IS STD_LOGIC_VECTOR(3 DOWNT0 0);
        TYPE memArray IS ARRAY(0 TO 15) OF cell;
        VARIABLE mem: memArray;
    BEGIN
        IF CE = '1' AND WR = '0' THEN      -- read
            D <= mem(TO_INTEGER(UNSIGNED(A)));
        ELSIF CE = '1' AND WR = '1' THEN -- write
            mem(TO_INTEGER(UNSIGNED(A))) := D;
        ELSE -- not enabled or invalid
            D <= (OTHERS=>'Z');
        END IF;
    END PROCESS;
END Behavioral;

```

Representing a RAM memory by an array of bytes is a perfectly reasonable behavioural model, but it won't necessarily synthesise into a memory (it might synthesise into a large block of registers or latches!).

ROM: “Read-Only” Memory


- Nonvolatile memory
- Can be read from but not written to, by a processor in an embedded system.
- Traditionally written to, “programmed”, before inserting to embedded system.
- Usage
 - store software program for general-purpose processor;
 - program instructions can be one or more ROM words;
 - store constant data needed by system;
 - implement combinational circuit.

Outline

- Overview of A Microprocessor
- Datapath
- Control Unit
- Memory
- Lab ALU

Lab ALU

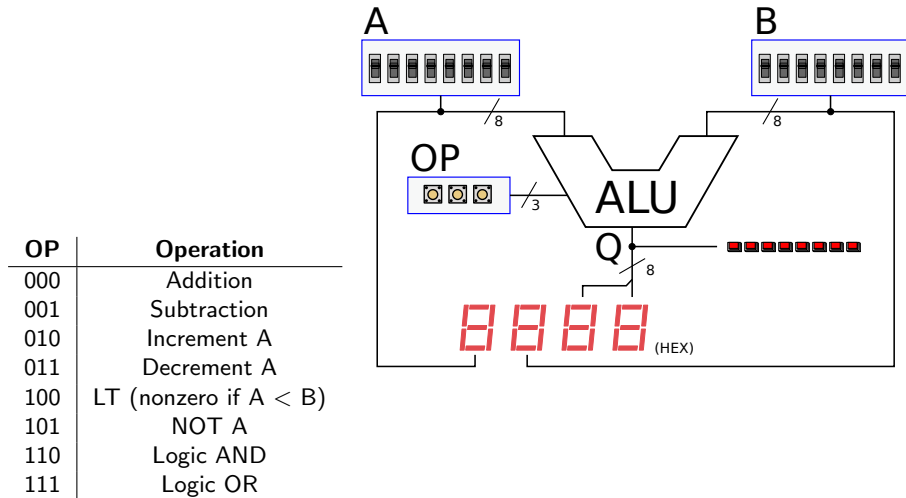Implement (using behavioural style) an ALU performing the operations in the table on the left and test it on the Basys 3 board using the layout on the right:



Thank you
for your attention



Questions?

Microprocessor Design

School of Computer Science and Electronic Engineering
University of Essex (UK)

CE339/CE869 - Lecture 7
Jan 2020